

Application Note***THAN0201_Rev.2.00_E***

THC63LVDM83D/THC63LVDF(R)84C

Application Note

System Diagram and PCB Design Guideline

Date	Revision
2015/08/04	Rev.1.00_E
2015/10/21	Rev.1.10_E
2015/11/04	Rev.2.00_E

Contents

Contents	2
1. TTL Data Timing Diagram	3
2. LVDS Data Timing Diagram	4
3. Examples of System Diagrams	5
4. Note	8
5. PCB Design Guideline.....	9
Notices and Requests	10

1. TTL Data Timing Diagram

Figure 1 and Table 1 shows the THC63LVDM83D TTL data input example for XGA(1024x768).

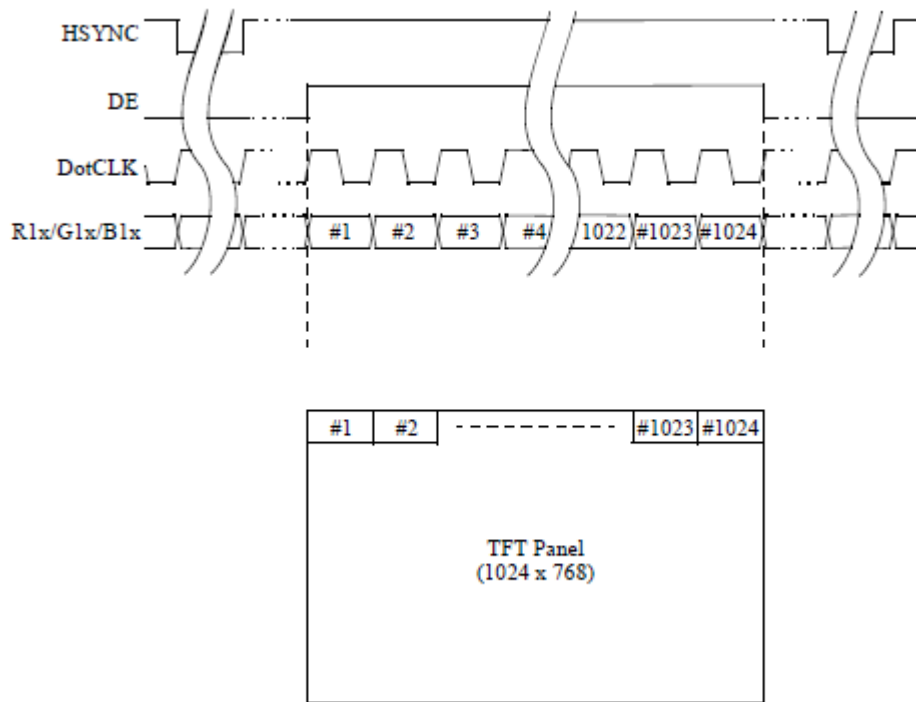


Figure 1. THC63LVDM83D TTL data timing diagram example (XGA, 1024x768)

Table 1. RGB ordering

	Red	Green	Blue
MSB	R7	G7	B7
	R6	G6	B6
	R5	G5	B5
	R4	G4	B4
	R3	G3	B3
6bit LSB	R2	G2	B2
	R1	G1	B1
8bit LSB	R0	G0	B0

2. LVDS Data Timing Diagram

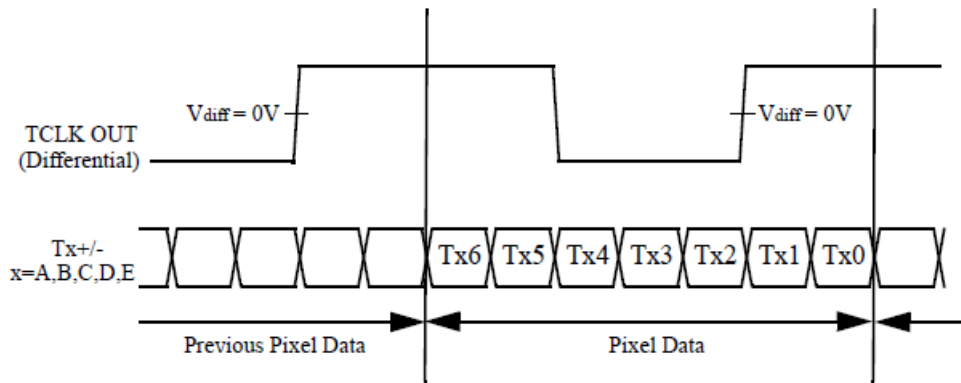


Figure 2. THC63LVDF(R)84C LVDS data input timing diagram

Table 2. THC63LVDM83D/THC63LVDF(R)84C Pixel Data Assignment (6bit, 8bit Application)

	6bit	8bit
TA0	R2	R2
TA1	R3	R3
TA2	R4	R4
TA3	R5	R5
TA4	R6	R6
TA5	R7	R7
TA6	G2	G2
TB0	G3	G3
TB1	G4	G4
TB2	G5	G5
TB3	G6	G6
TB4	G7	G7
TB5	B2	B2
TB6	B3	B3
TC0	B4	B4
TC1	B5	B5
TC2	B6	B6
TC3	B7	B7
TC4	Hsync	Hsync
TC5	Vsync	Vsync
TC6	DE	DE
TD0	-	R0
TD1	-	R1
TD2	-	G0
TD3	-	G1
TD4	-	B0
TD5	-	B1
TD6	-	N/A

Note: For 6bit application, use TA-TC channel and open TD+/- pin.


3. Examples of System Diagrams

1) 8bit TTL/CMOS Input(8 to 112MHz)

Example:

THC63LVDM83D: Falling edge/Normal Swing

THC63LVDF84C: Falling edge

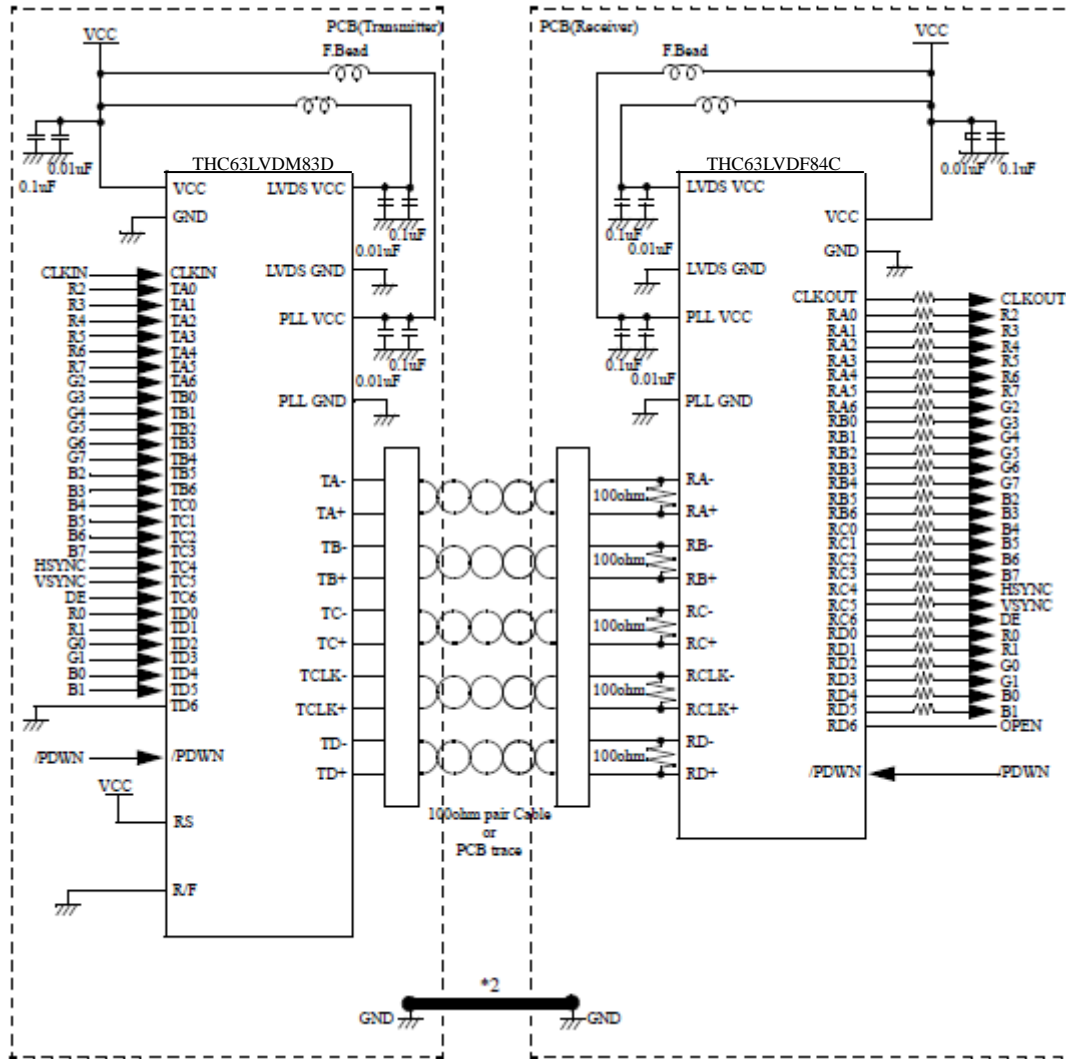

*1: If RS pin is tied to VCC, LVDS swing is 350mV.
 If RS pin is tied to GND, LVDS swing is 200mV.

*2: Connect each PCB GND


Figure 3. System Diagram Example (8bit TTL/CMOS Input)

2) 8bit Small Swing Input(8 to 112MHz)


Example:

THC63LVDM83D: Small Swing input/Falling edge

THC63LVDF84C: Falling edge

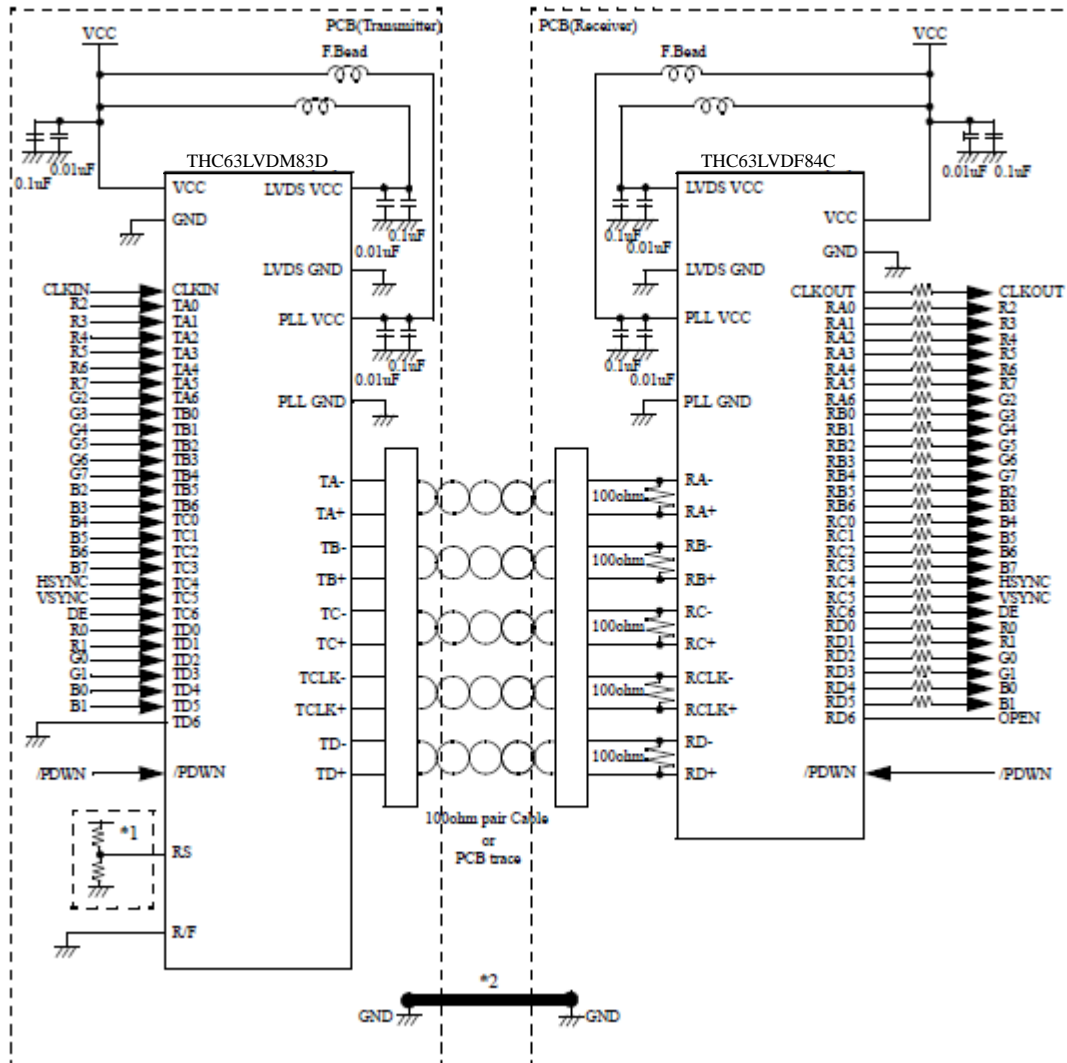

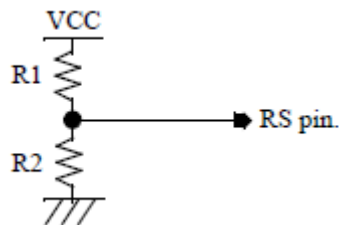*1: RS pin acts as VREF input pin when input voltage is set to half of high level signal input.



*2: Connect each PCB GND


Figure 4. System Diagram Example (8bit Small Swing Input)

3) 6bit TTL/CMOS Input(8 to 112MHz)

Example:

THC63LVDM83D: Falling edge/Normal Swing

THC63LVDF84C: Falling edge

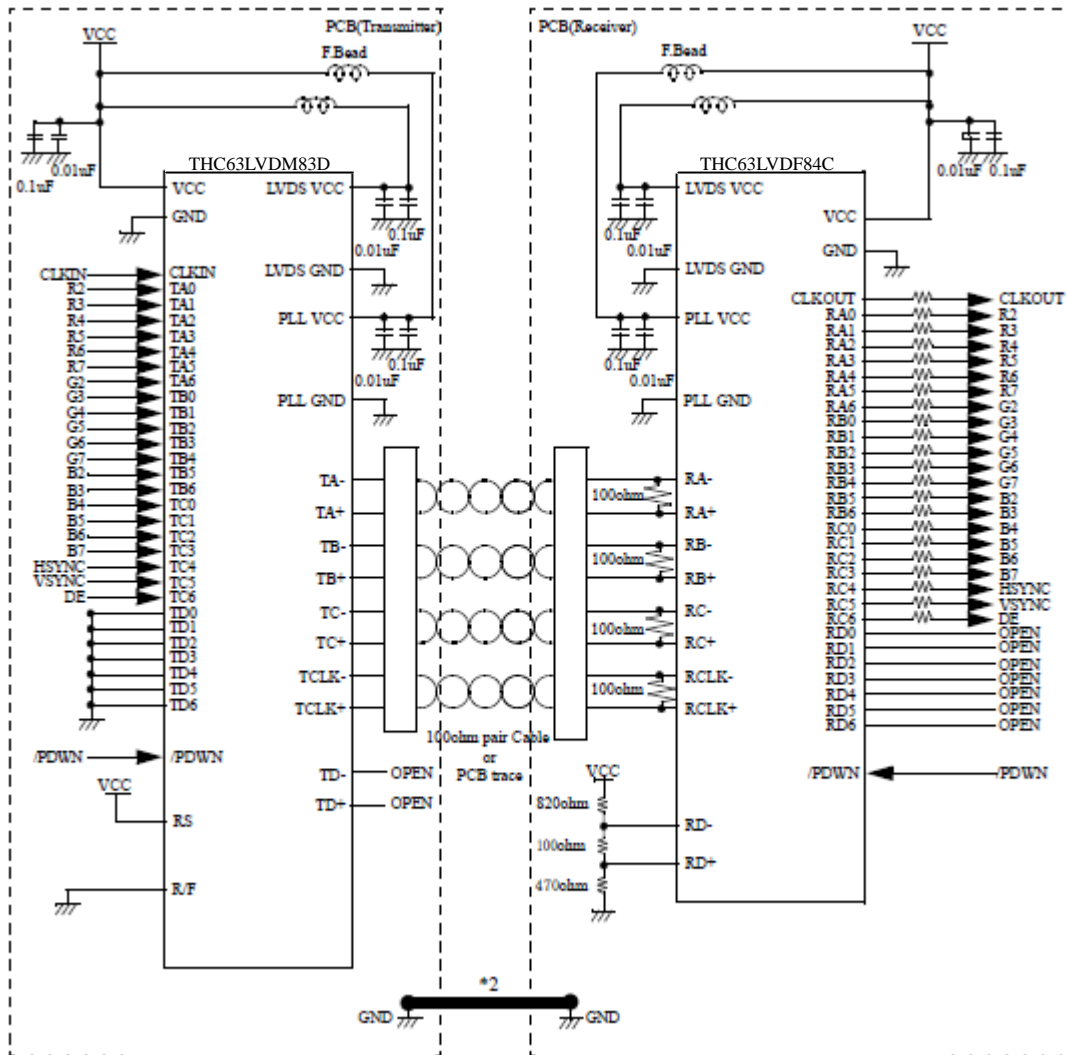

*1: If RS pin is tied to VCC, LVDS swing is 350mV.
 If RS pin is tied to GND, LVDS swing is 200mV.

*2: Connect each PCB GND

Figure 5. System Diagram Example (6bit TTL/CMOS Input)

4. Note

1) Power On Sequence

Power on THC63LVDM83D after THC63LVDF(R)84C is powered on.

2) Cable Connection and Disconnection

Don't connect and disconnect the LVDS cable, when the power is supplied to the system.

3) GND Connection

Connect the each GND of the PCB which THC63LVDM83D and THC63LVDF(R)84C on it. It is better for EMI reduction to place GND cable as close to LVDS cable as possible.

4) Multi Drop Connection

Multi drop connection is not recommended.

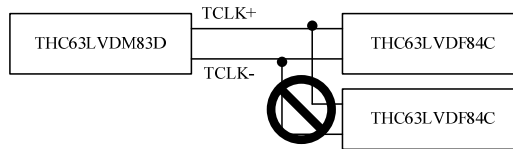


Figure 6. Multi Drop Connection Example (not recommended)

5) Asynchronous Use

Asynchronous use such as following systems is not recommended.

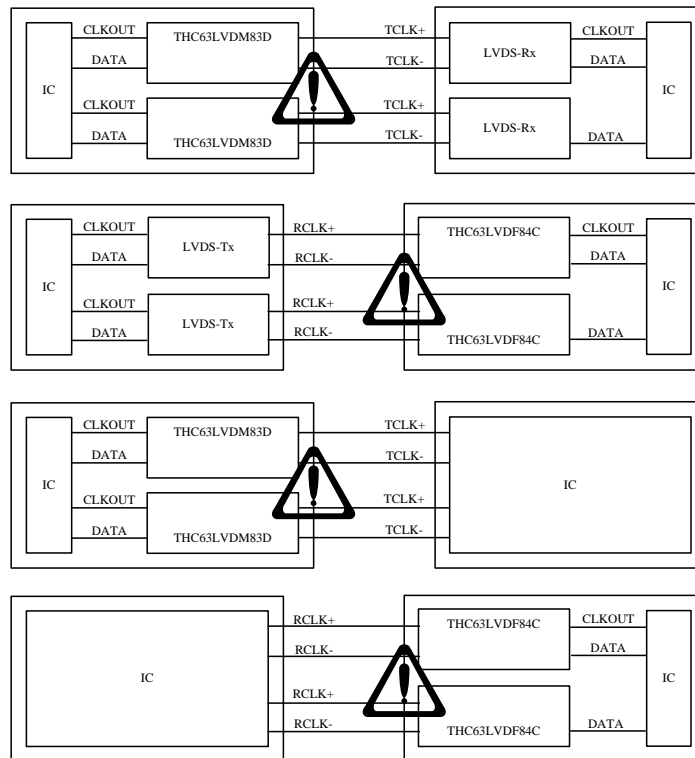


Figure 7. Asynchronous Use Examples (not recommended)

5. PCB Design Guideline

General Guideline

- Use 4 layer PCB (minimum).
- Locate by-pass capacitors adjacent to the device pins as close as possible.
- Make the loop minimum which consist of Power line and Gnd line.

LVDS Traces

- Interconnecting media between Transmitter and Receiver (i.e. PCB trace, connector, and cable) should be well balanced.(Keep all these differential impedance and the length of media as same as possible.).
- Minimize the distance between traces of a pair ($S1$) to maximize common mode rejection. See following figure.
- Place adjacent LVDS trace pair at least twice ($>2 \times S1$) as far away as much as possible.
- Avoid 90 degree bends.
- Minimize the number of VIA on LVDS traces.
- Match impedance of PCB trace, connector, media (cable) and termination to minimize reflections (emissions) for cabled applications (typically 100ohm differential mode characteristic impedance).
- Place Terminal Resistor adjacent to the Receiver.

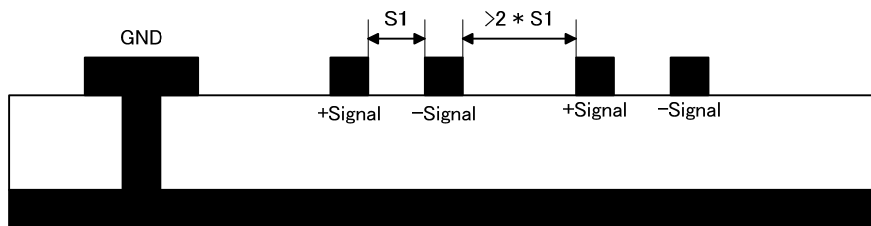


Figure 8. PCB Design Guideline

Notices and Requests

1. The product specifications described in this material are subject to change without prior notice.
2. The circuit diagrams described in this material are examples of the application which may not always apply to the customer's design. We are not responsible for possible errors and omissions in this material. Please note if errors or omissions should be found in this material, we may not be able to correct them immediately.
3. This material contains our copyright, know-how or other proprietary. Copying or disclosing to third parties the contents of this material without our prior permission is prohibited.
4. Note that if infringement of any third party's industrial ownership should occur by using this product, we will be exempted from the responsibility unless it directly relates to the production process or functions of the product.
5. Product Application 5.1 Application of this product is intended for and limited to the following applications: audio-video device, office automation device, communication device, consumer electronics, smartphone, feature phone, and amusement machine device. This product must not be used for applications that require extremely high-reliability/safety such as aerospace device, traffic device, transportation device, nuclear power control device, combustion chamber device, medical device related to critical care, or any kind of safety device. 5.2 This product is not intended to be used as an automotive part, unless the product is specified as a product conforming to the demands and specifications of ISO/TS16949 ("the Specified Product") in this data sheet. THine Electronics, Inc. ("THine") accepts no liability whatsoever for any product other than the Specified Product for it not conforming to the aforementioned demands and specifications. 5.3 THine accepts liability for demands and specifications of the Specified Product only to the extent that the user and THine have been previously and explicitly agreed to each other.
6. Despite our utmost efforts to improve the quality and reliability of the product, faults will occur with a certain small probability, which is inevitable to a semi-conductor product. Therefore, you are encouraged to have sufficiently redundant or error preventive design applied to the use of the product so as not to have our product cause any social or public damage.
7. Please note that this product is not designed to be radiation-proof.
8. Testing and other quality control techniques are used to this product to the extent THine deems necessary to support warranty for performance of this product. Except where mandated by applicable law or deemed necessary by THine based on the user's request, testing of all functions and performance of the product is not necessarily performed.
9. Customers are asked, if required, to judge by themselves if this product falls under the category of strategic goods under the Foreign Exchange and Foreign Trade Control Law.
10. The product or peripheral parts may be damaged by a surge in voltage over the absolute maximum ratings or malfunction, if pins of the product are shorted by such as foreign substance. The damage s may cause a smoking and ignition. Therefore, you are encouraged to implement safety measures by adding protection devices, such as fuses.

THine Electronics, Inc.

sales@thine.co.jp